

## OPEN CIRCUIT AND LOAD CHARACTERISTICS OF DC SHUNT GENERATOR

AIM:

To draw the open circuit and load characteristics of DC shunt generator.

APPARATUS REQUIRED:

Laptop with internet connection

THEORY:

DC generator converts mechanical energy into electrical energy.

DC generator works on the principle of Faraday's Law. It states that "When a conductor cuts the magnetic flux and e.m.f is induced."

The field winding and armature windings are connected in parallel in the shunt generator.

OPEN CIRCUIT CHARACTERISTICS:-

It is also known as magnetisation characteristics or no load characteristics. It is a graph drawn between open circuit voltage ( $E_o$ ) and field current ( $I_f$ ).

### Load circuit characteristics

It is a graph drawn between load voltage ( $V_L$ ) and load current ( $I_L$ ). It is also known as external characteristics.

### PROCEDURE:

#### OPEN circuit characteristics:-



1. connections are made as per the circuit diagram.
2. switch on the supply and note down the readings (Voltage and current)
3. By varying the field rheostat different values of open circuit voltage and field current are noted.
4. Plot the graph between open circuit voltage and field current.

#### Load characteristics:-

1. connections are made as per the circuit diagram.
2. switch on the supply and note the no load voltage and current.
3. By connecting different nodes, different values of load voltage and note current are noted.

## OPEN CIRCUIT CHARACTERISTICS


## CIRCUIT DIAGRAM:

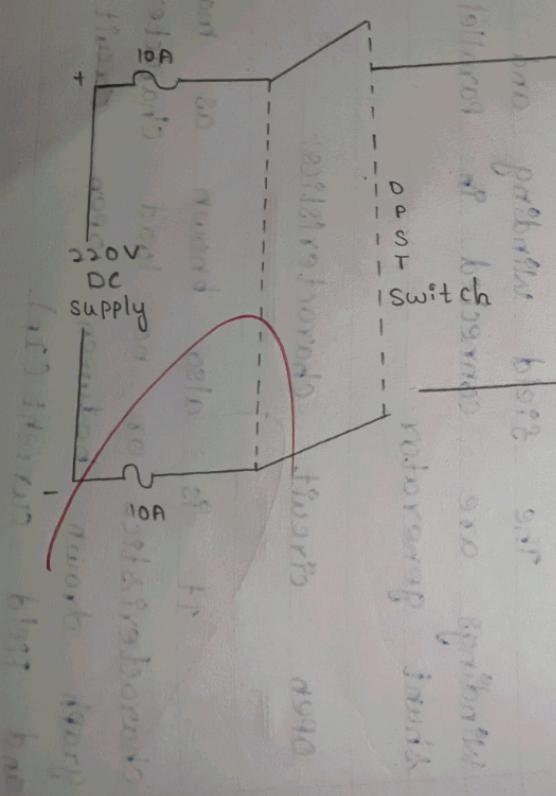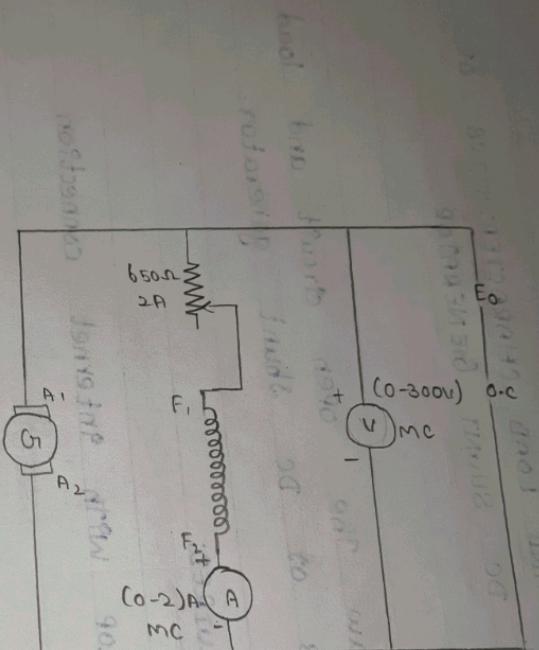


4. Plot the graph between load voltage and load current.



### MODEL GRAPH

open circuit characteristics

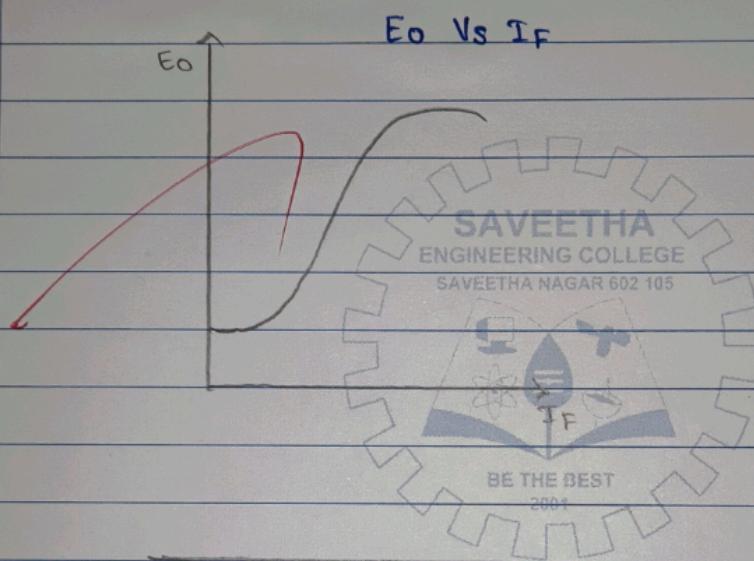

S.NO	VOLTAGE (V)	CURRENT (A)
1	115	0.16
2	120	0.18
3	126	0.20
4	129	0.21
5	133	0.23
6	135	0.24
7	138	0.28
8	142	0.30

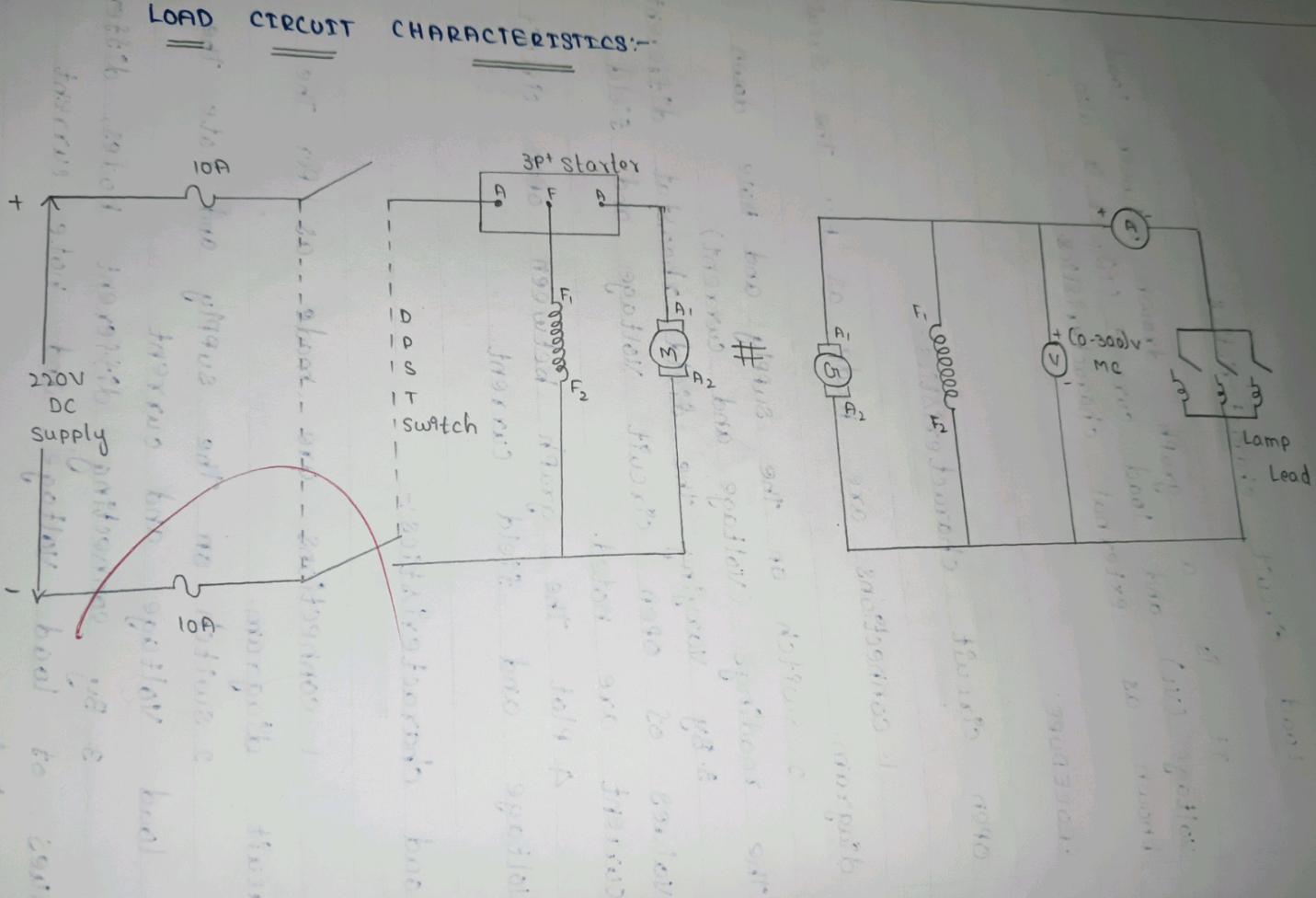

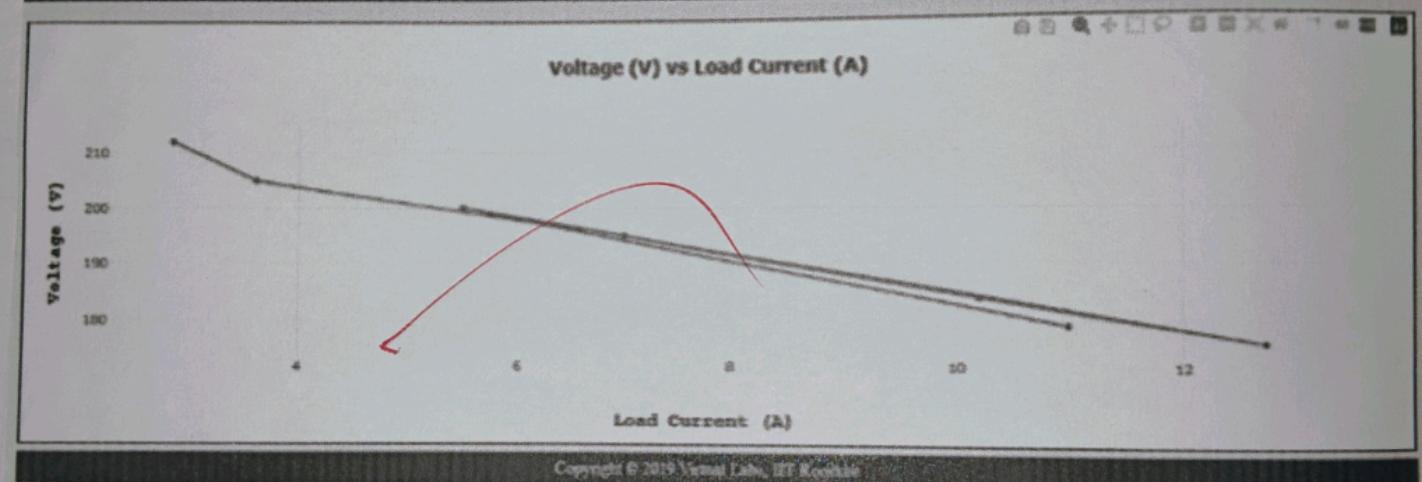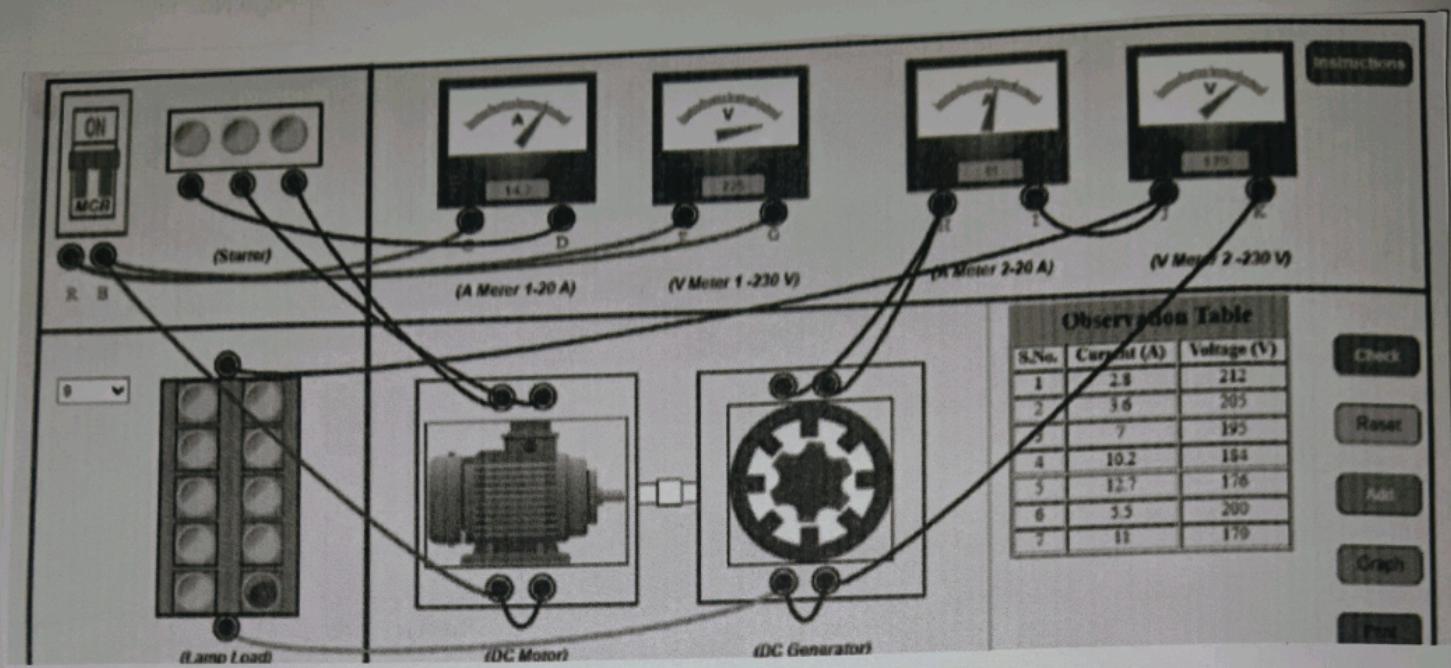

Copyright © 2019 Virtual Lab, IIT Madras

81.0

60.0

160

20.0

10.0

82.0

60.0

0.0

10.0

160

20.0

82.0

60.0

81.0

C

E


A

D

d

F


o

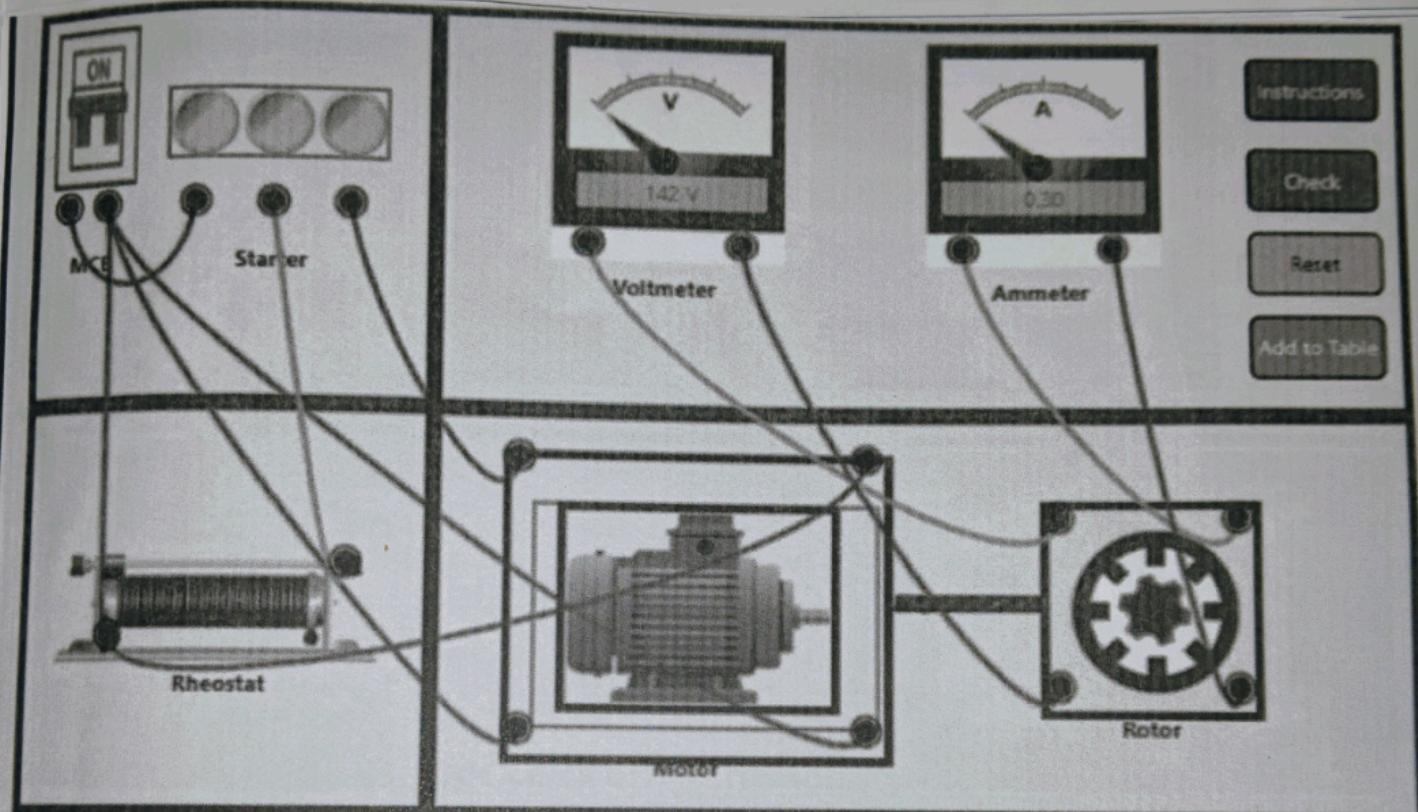

OBSERVATION TABLE

S.No.	Voltage (V)	Current (A)
1	115	0.16
2	120	0.18
3	126	0.20
4	129	0.21
5	133	0.23
6	135	0.24
7	138	0.28
8	142	0.30
9	0	0

Current (A) vs Voltage (V)

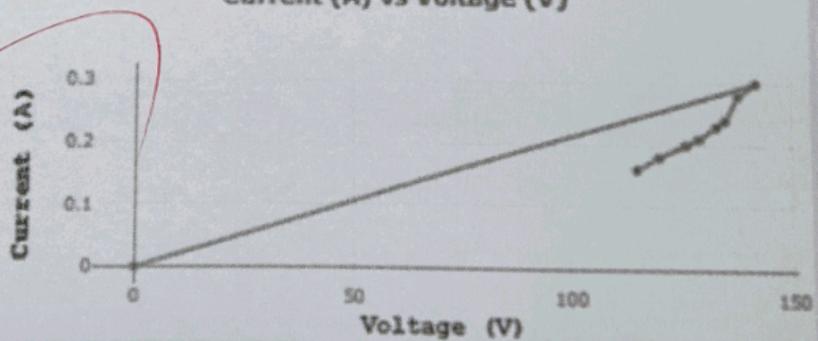

MODEL GRAPH

## Load characteristics

Load voltage

A graph showing Load Voltage ( $V_L$ ) decreasing as Load current ( $I_L$ ) increases. The vertical axis is labeled  $V_L$  (V) and the horizontal axis is labeled  $I_L$  (A).

Load curve

 $I_L$  (A)

S.NO	CURRENT(A)	VOLTAGE(V)
1	1.2	220
2	2.8	212
3	3.2	208
4	3.6	205
5	5.5	200
6	7.7	195

RESULT:

Thus the open circuit and load characteristics of DC shunt generator were verified successfully.

OPEN CIRCUIT CHARACTERISTIC


X-axis 1cm = 0.02A  
Y-axis 1cm = 10V

$E_O$   
(V)

160  
150  
140  
130  
120  
110  
100  
90  
80  
70  
60  
50  
40  
30  
20  
10

0 0.02 0.04 0.06 0.08 0.10 0.12 0.14 0.16 0.18 0.20 0.22 0.24 0.26 0.28 0.30

IF(A)

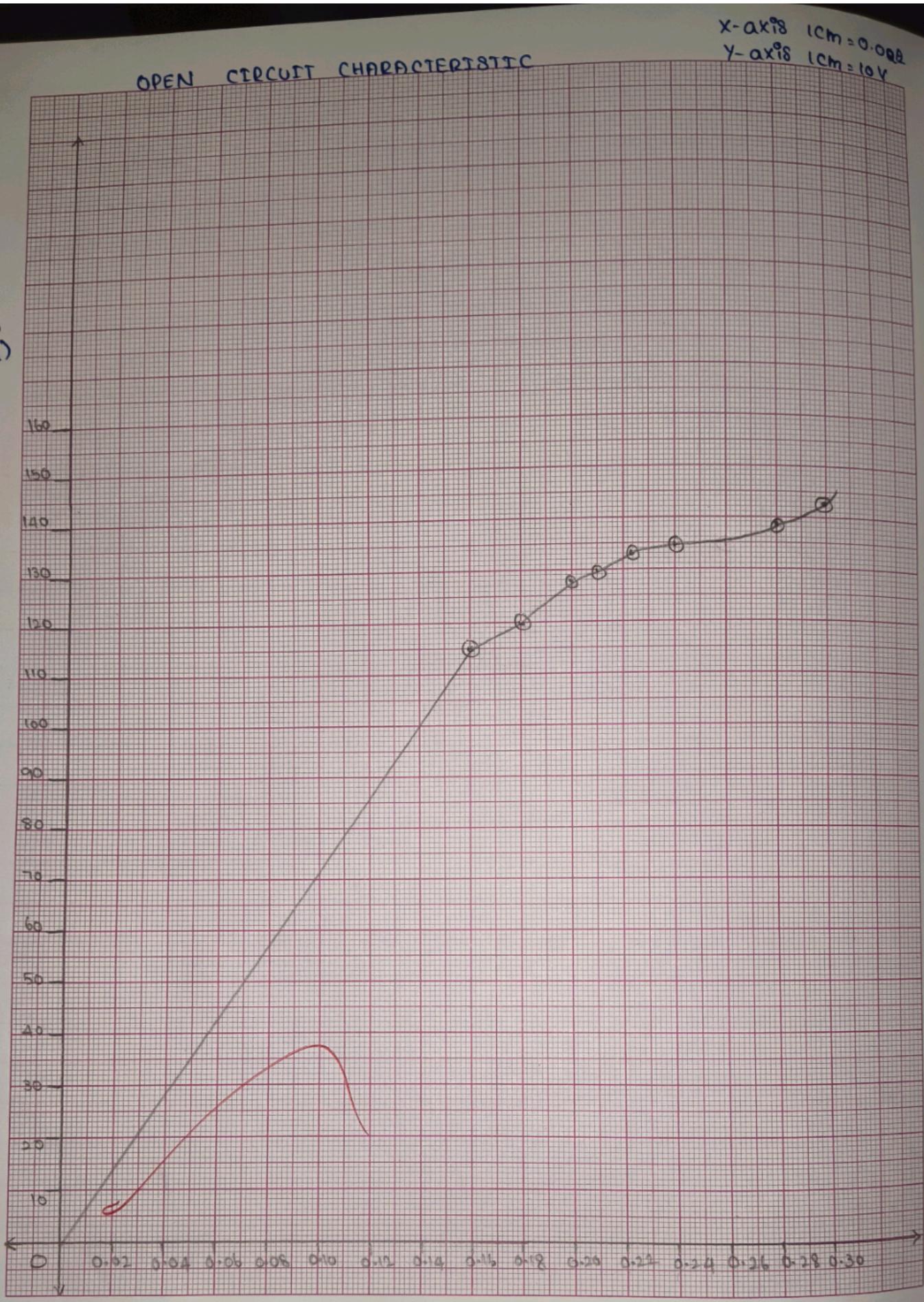

Expt. No. 6

LOAD CHARACTERISTIC

